

# Lab Report No 4

## Digital Logic Design



### Submitted By:

Abdul Ahad

22-CS-071

Muhammad Afzal

22-CS-035

Muhammad Zain Ali

22-CS-015

Faisal Khan

22-CS-039

Bilal Asghar

22-CS-107

### Submitted to:

Engr. Bushra Fiaz

### Dated:

Week 01

Department of Computer Science,  
HITEC University, Taxila

## Lab Task No 1:

### Solution:

#### Brief description (3-5 lines)

- Simplify the Boolean function  $F(A,B,C) = \Sigma(0,1,2,4,6,7)$  using 3-variable K-Map, implement the minimized and original circuit with Logisim and digital logic trainer and compare the results


#### The code


		B, C			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	1	1

$\bar{A}\bar{B} + \bar{C} + AB$



#### The results (Screenshot)

##### Original:

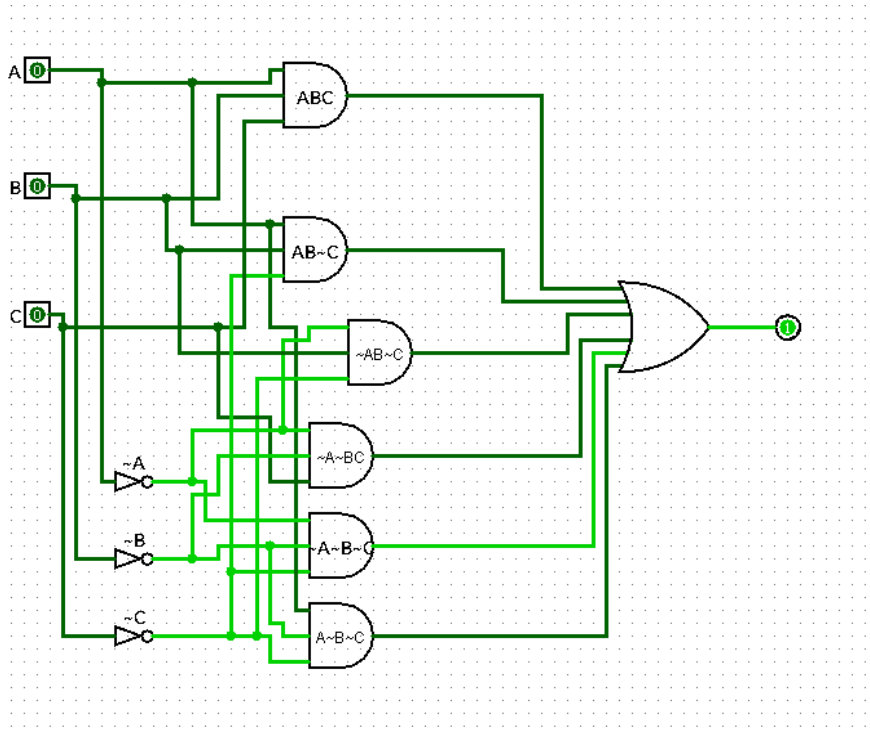

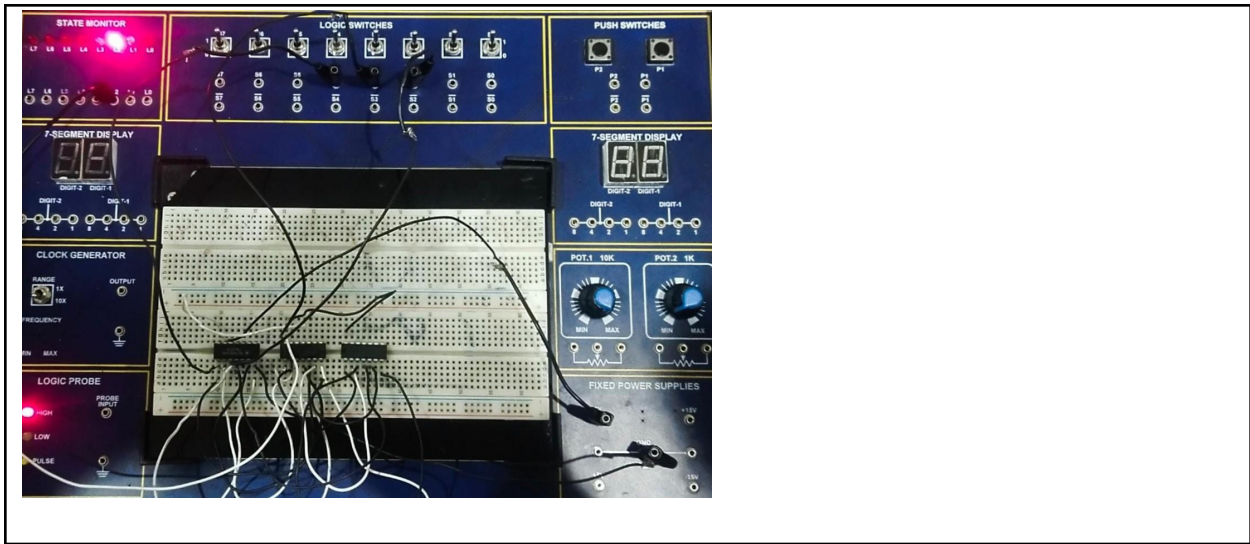

**Simplified:**

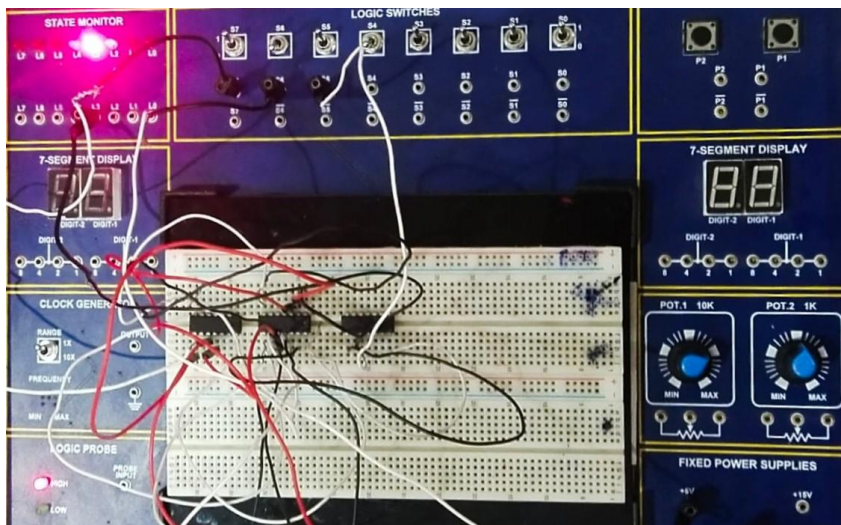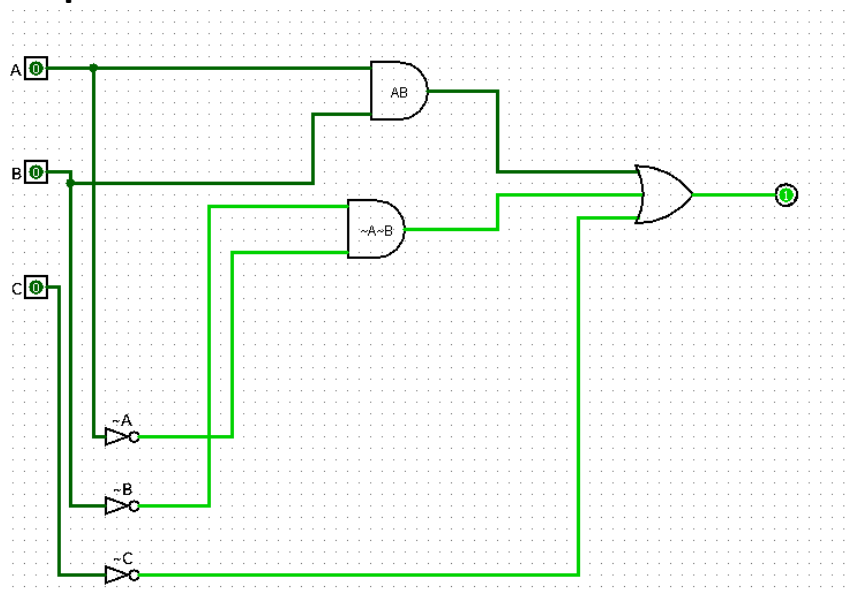

## Lab Task No 2:

### Solution:


**Brief description (3-5 lines)**

- Fill the truth table for both the equations and compare with the Observed value to verify the equation. Remember, results from both tables should be the same.

**Original:**

A	B	C	A'B'C'	A'B'C	AB'C'	ABC	ABC'	A'BC'	F(A, B, C)= A'B'C' + A'B'C + AB'C' + ABC+ABC'+A'BC'	
									Calculated Values	Observed Value
0	0	0	1	0	0	0	0	0	1	1
0	0	1	0	1	0	0	0	0	1	1
0	1	0	0	0	0	0	0	1	1	1
0	1	1	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	1	1
1	1	1	0	0	0	1	0	0	1	1

A	B	C	x
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

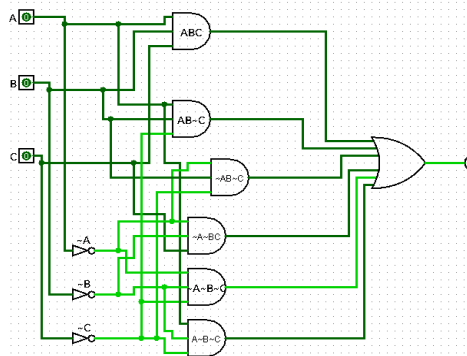

# Minimized:

A	B	C	AB	A'B'	C'	F(A,B,C) = AB + A'B' + C'	
						Calculated Values	Observed Value
0	0	0	0	1	1	1	1
0	0	1	0	1	0	1	1
0	1	0	0	0	1	1	1
0	1	1	0	0	0	0	0
1	0	0	0	0	1	1	1
1	0	1	0	0	0	0	0
1	1	0	1	0	1	1	1
1	1	1	1	0	0	1	1

A	B	C	x
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

