

# Lab Report No 7

## Digital Logic Design



### Submitted By:

Abdul Ahad

22-CS-071

Muhammad Afzal

22-CS-035

Muhammad Zain Ali

22-CS-015

Faisal Khan

22-CS-039

Bilal Asghar

22-CS-107

### Submitted to:

Engr. Bushra Fiaz

### Dated:

Week 07

Department of Computer Science,  
HITEC University, Taxila

## Half Adder:

### Solution:


#### Brief description

Implement and verify the Half Adder Boolean expression by basic logic gates on trainer board and simulate the circuit with Logisim.


#### The code

Half Adder is combinational logic circuit that generates the sum of two binary numbers (each having 1-bit length). The logic circuit has two inputs and two outputs

#### The results (Screenshot)

 

A	B	x	y
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

A	B	x	y
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## Full Adder:

### Solution:


#### Brief description

Implement and verify the Full Adder Boolean expression by basic logic gates on trainer board and simulate the circuit with Logisim.


#### The code

Full Adder is combination logic circuit that performs the sum of 3 input binary numbers, (each having 1-bit length). Two of the binary input variables are x and y represent the two significant bits to be added the third input z, represents the carry from previous lower significant position.

#### The results (Screenshot)

 

A	B	C	x	y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

A	B	C	x	y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1